



Subject :- BEE

Experiment / Tutorial / Assignment No. :- 01

Page :- 01

Date :- 24/01/2022

* Experiment NO. 01 : MESH AND NODAL ANALYSIS *

Aim : To perform mesh and Nodal analysis for the given Circuit.

Objective : After performing the practical, the learner will be able to :

PRO 1 : Implement the given Circuit On breadboard

PRO 2 : Explain the basic Concept of Mesh and Nodal Analysis

PRO 3 : Calculate Voltage and Current across different Component in circuit.

Apparatus :

Digital multimeter, Power Supply, resistors, bread board, Wires.

Procedure :


PRO 1 : 1.1 Construct the circuit as shown in the Circuit diagram 1.

PRO 2 : 2.1 Measure the Current through resistors.


PRO 3 : 3.1 Calculate the theoretical value for Current through all resistor Using Mesh analysis.
3.2 Compare it with the Practical Value.



Electric circuit diagram :-

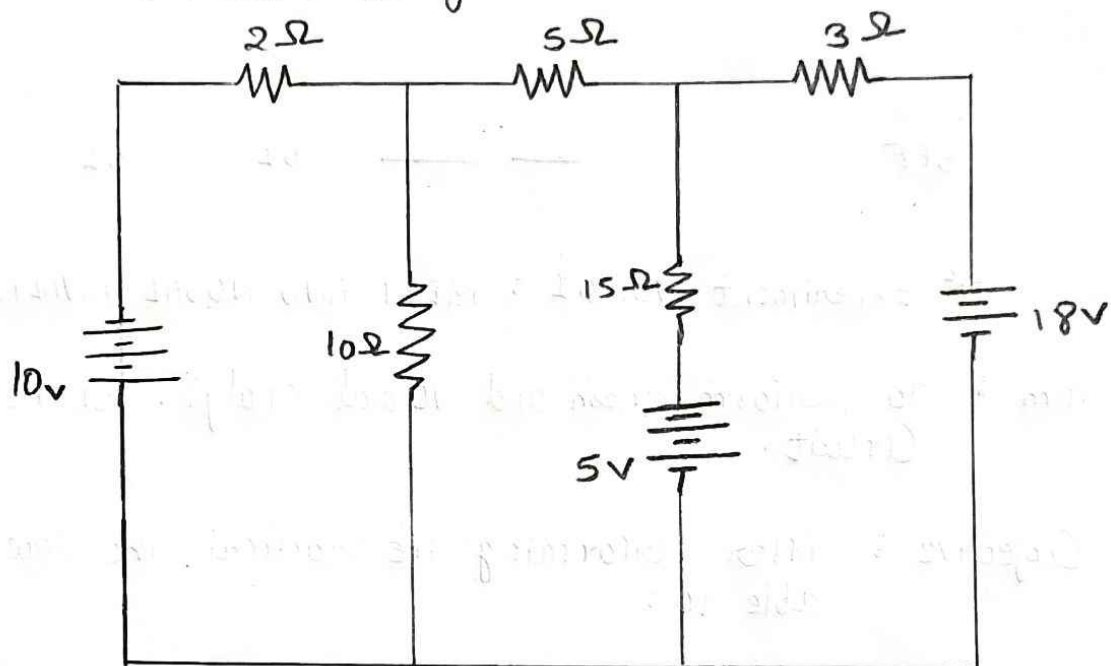

PRACTICAL CIRCUIT DIAGRAM:-

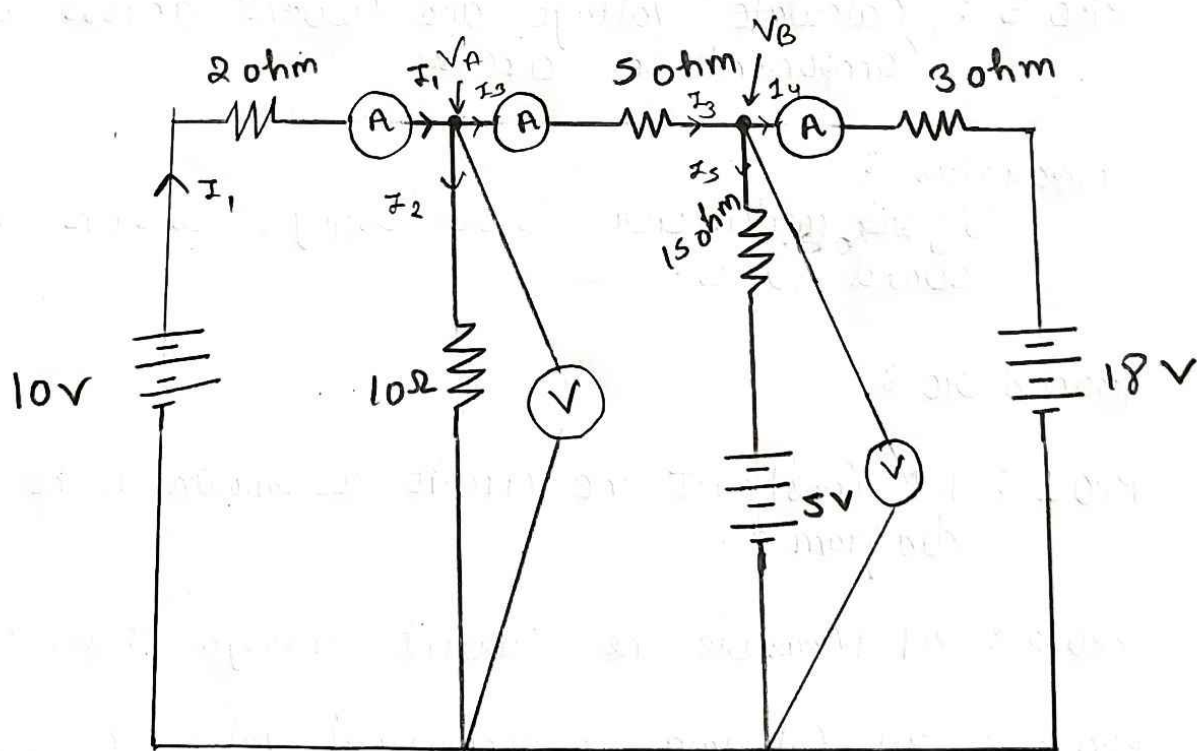



Zagda Singh Charitable Trust's (Regd.)

THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193rd in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Website : www.tcetmumbai.in

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 1

Page :- 02

Date :- 24/01/2022

PRO 1 : 1.2 Construct the Circuit as shown in the diagram 2

PRO 2 : 2.2 Measure the voltage across all nodes

PRO 3 : 3.3 Calculate the theoretical value for the voltage across all nodes using Nodal Analysis
3.4 Compare it with the practical value.


Result and Discussion :

PRO 1 : Breadboard is easy to use for creating temporary prototypes and experimenting with circuit design.

PRO 2 : Mesh and Nodal Analysis is used for measuring the current and voltage of the circuit.

PRO 3 : Current is measured using Mesh analysis and voltage across any resistance can be calculated. is measured using Nodal Analysis.

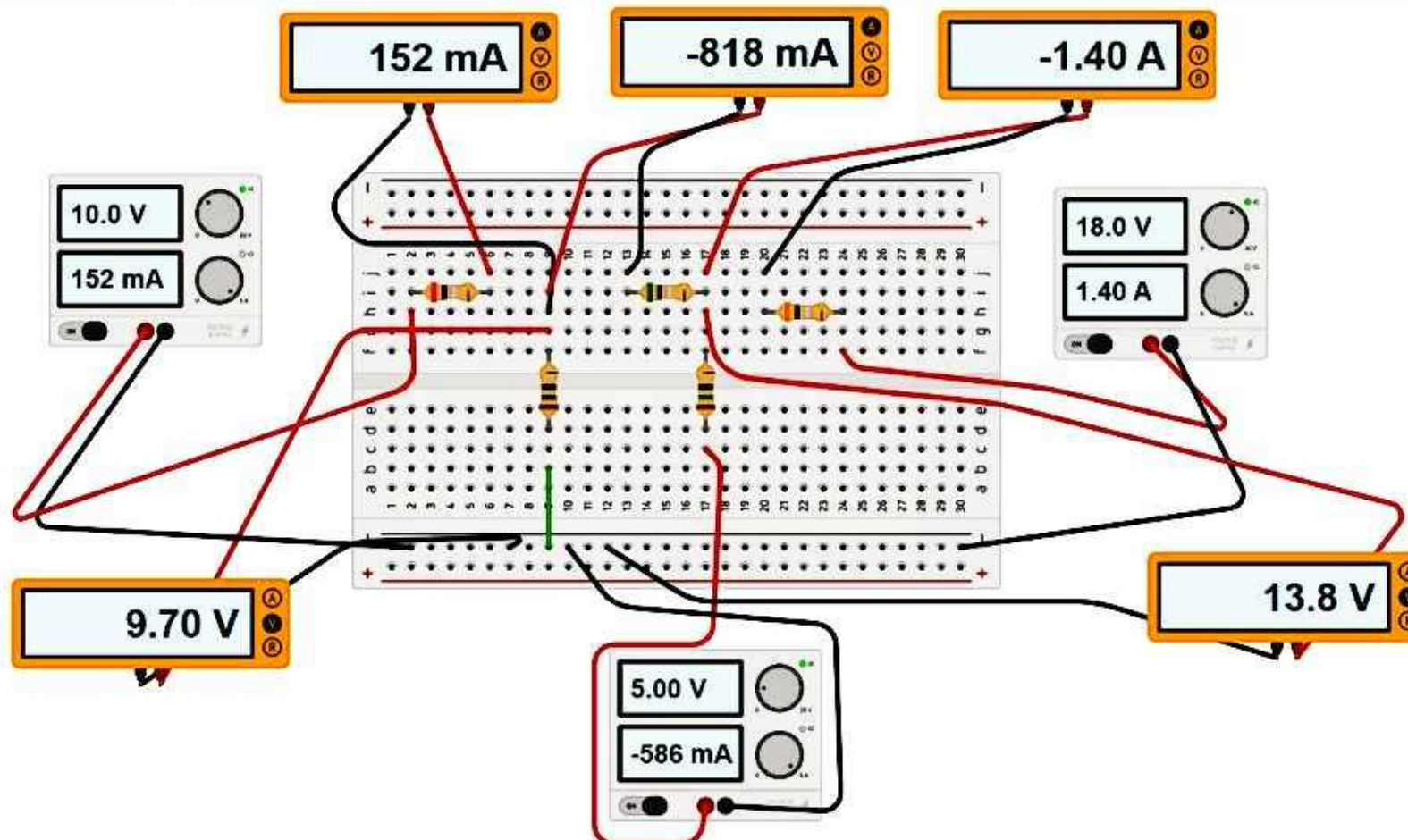Conclusion : Hence by applying mesh and nodal analysis current and voltage across any resistance can be calculated.



- Components: Basic
- Search
- Diode
 - Photoresistor
 - Ultrasonic Distance Sensor
 - PIR Sensor
 - Piezo
 - Temperature Sensor [TMP36]
 - Multimeter

* mesh Analysis

| I_1 | | I_2 | | I_3 | |
|------------|----------|------------|----------|------------|----------|
| calculated | observed | calculated | observed | calculated | observed |
| 0.15A | 0.15A | -0.818A | -0.818A | -1.40A | -1.40A |

Calculation :-

By applying KVL in loop-I

$$10 - 2I_1 - 10(I_1 - I_2) = 0$$

$$\therefore -2I_1 - 10I_1 + 10I_2 = -10$$

$$\therefore 12I_1 - 10I_2 = 10 \dots \dots (i)$$

By applying KVL in loop-II

$$-5I_2 - 15(I_2 - I_3) - 5 + 10(I_1 - I_2) = 0$$

$$\therefore -5I_2 - 15I_2 + 15I_3 - 5 + 10I_1 - 10I_2 = 0$$

$$\therefore 10I_1 - 30I_2 + 15I_3 = 5$$

$$\therefore 2I_1 - 6I_2 + 3I_3 = 1 \dots \dots (ii)$$

By applying KVL in loop-III

$$-3I_3 - 18 + 15(I_2 - I_3) + 5 = 0$$

$$-3I_3 - 18 + 15I_2 - 15I_3 = 0$$

$$15I_2 - 18I_3 = 13 \dots \dots (iii)$$

$$\therefore I_1 = \frac{5}{33} = 0.1515$$

$$\therefore I_2 = -\frac{9}{11} = -0.8182$$

$$\therefore I_3 = -\frac{139}{99} = -1.404$$

* Nodal Analysis :-

| V_A | | V_B | |
|------------|----------|------------|----------|
| calculated | observed | calculated | observed |
| 9.69V | 9.70V | 13.78V | 13.80V |

calculation :

Applying KCL to node A

$$I_1 = I_2 + I_3$$

$$\frac{10 - V_A}{20} = \frac{V_A - 0}{10} + \frac{V_A - V_B}{5}$$

$$4V_A - V_B = 25 \quad \dots \dots (i)$$

Applying KCL to node B

$$I_3 = I_4 + I_5$$

$$\frac{V_A - V_B}{5} = \frac{V_B - 18}{3} + \frac{V_B - 5}{15}$$

$$3V_A - 19V_B = -95$$

$$V_A = \frac{320}{33} = 9.697 \text{ V} \quad (ii)$$

$$V_B = \frac{455}{33} = 13.79 \text{ V}$$



Zagdu Singh Charitable Trust's (Regd.)

THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193rd in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Website : www.tcetmumbai.in

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 1 Page :- 03 Date : 24/01/2022

Quiz

Q.1) What is use of Breadboard and multimeter?

Ans → Breadboard is used to build and test circuit's quickly before finalizing any circuit design and multimeter is used to measure electrical charging of voltage, current and resistor.

Q.2) Why do you require mesh and nodal analysis?

Ans → nodal analysis used to determine node voltage by solving KCL equation for the incoming and outgoing voltage at each node. mesh analysis used to determine current across each component in loop.

Q.3) Define voltage and current.

Ans → Voltage → It's difference in potential between points

Current → It is rate at which charge is flowing through circuit.



Zagdu Singh Charitable Trust's (Regd.)

THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193rd in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Website : www.tcetmumbai.in

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 01

Page :- 04

Date :- 24/01/2022

| Objective | PRO 1 | PRO 2 | PRO 3 | Total Score | ES & H Department |
|--------------------------------------|-------|-------|-------|----------------|-----------------------|
| Weight points | 20 | 30 | 30 | | Date of Performance:- |
| Score | | | | | Date of Correction:- |
| Earned points (EP) = Total score/100 | | | | | Roll No. → 29 |
| = | | | | | Marks : — /100 |
| | | | | | Signature → |